

## BASIC CIRCUIT ELEMENTS AND THEORY

### INTRODUCTION TO CIRCUIT ELEMENT:

Electric circuit is an inter connection of electric elements.

- Charge is electrical property of atomic particles.  
Unit → Coulombs
- Charge on electron =  $-1.6 \times 10^{-19}\text{C}$
- Current is time rate of change of charge.

$$I = \frac{dq}{dt} \quad \text{or} \quad q = \int_0^t I dt$$

$$\text{Unit} \rightarrow \frac{\text{C}}{\text{sec}} \quad \text{or} \quad \text{Amp}$$

- Voltage is the energy required to move a charge from one point to another point.

$$V = \frac{dW}{dq}$$

$$\text{Unit} \rightarrow \frac{\text{J}}{\text{C}} \quad \text{or} \quad \text{Volt}$$

- Power is the time rate of change of energy.

$$P = \frac{dW}{dt} \quad \text{or} \quad W = \int P dt$$

$$\text{Unit} \rightarrow \frac{\text{Joule}}{\text{sec}}$$

### Classification of circuit element:-

#### (i) Unilateral and Bilateral element:-

If the element property and characteristic does not change with direction of current, then the element is called bilateral element; otherwise unilateral element.

#### (ii) Linear and non linear element:-

If the element satisfy homogeneity and additivity property then element is called linear element, otherwise non linear.

#### (iii) Active and passive Elements:

Active Elements: When the element is capable of delivering the energy, it is called active element.


**Example:** Voltage source, Current source, Transistor, Diode, Op-amp etc

Passive Elements: When the element is not capable of delivering the energy, it is called passive element.

Example: Resistance, capacitor, inductor etc.

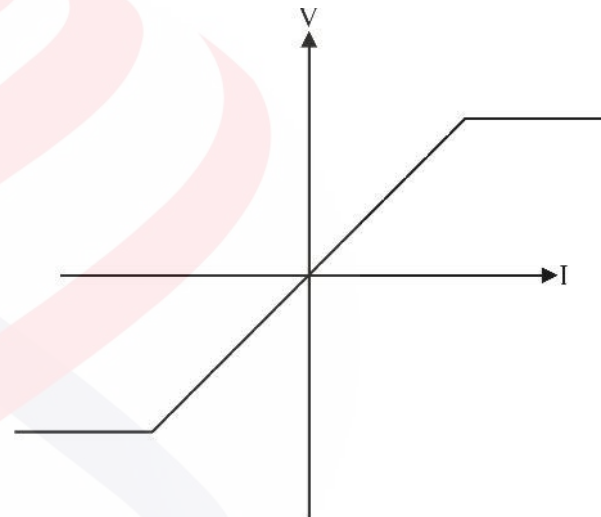**Example:** Identify whether the element is:

- Linear or non linear
- Active or passive
- Bilateral or unilateral



Solution:-

- Nonlinear, as slope is not constant.
- Passive, as  $V/I$  is +ve in both quadrants.
- Bilateral, as characteristic is identical in opposite quadrant.

### 1. Resistance:

Ohm's law:- Voltage  $V$  across a resistor is directly proportional to the current  $i$  flowing through the resistor

$$\Rightarrow V \propto i$$

$V = iR$ , This constant of proportionality is called 'resistance'.

$\Rightarrow$  Case 1:- When  $R = 0 \rightarrow$  short circuit

$$\text{Then } V = 0 \text{ and } I = \infty$$

Case 2:- When  $R = \infty \rightarrow$  Open circuit

$$\text{Then } V = \infty \text{ and } I = 0$$

**Key Points:**

- Power in resistor is given by


$$P = vi = i^2 R = \frac{v^2}{R}$$

- Energy is then determined as the integral of instantaneous power as :

$$E = \int_{t_1}^{t_2} P dt = R \int_{t_1}^{t_2} i^2 dt = \frac{1}{R} \int_{t_1}^{t_2} v^2 dt$$

- Resistor consumes energy and converts electrical energy into heat energy.
- Resistance depends on the geometry of material and also on nature of material as:

$$R = \dots \frac{l}{A}$$

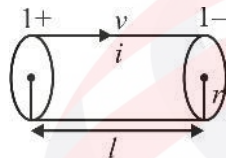

Where ... = Resistivity ( $\Omega.m$ )

... =  $1/\sigma$  ( $\sigma$  = conductivity)

Unit of conductivity: mho/m or Siemens/cm

- Resistivity of wire is materialistic property i.e. It does not vary with circuit geometry.
- Extension of wire result in increase in length & decrease in cross-sectional area therefore resistance of wire increases.
- When circuit is short circuit means,  $R = 0$ .  
When circuit is open,  $R = \infty$ .

**Example:** A conductor has a resistance of  $3\Omega$ . What is resistance of the same material? Which has one half the diameter and 4 times the length of the given conductor.

**EXP:**  $R_1 = \rho \frac{l_1}{A_1}$  ,  $R_2 = \rho \frac{l_2}{A_2}$

$$\Rightarrow \frac{R_2}{R_1} = \frac{l_2}{l_1} \frac{A_1}{A_2}$$

Now  $A_1 = \frac{\pi D_1^2}{4}$  ,  $A_2 = \frac{\pi D_2^2}{4}$

$$\Rightarrow \frac{A_1}{A_2} = \frac{D_1^2}{D_2^2} = \frac{D_1^2}{\left(\frac{D_1}{2}\right)^2} = 4 \text{ and}$$

$$l_2 = 4l_1 \Rightarrow \frac{l_2}{l_1} = 4$$

$$\Rightarrow \frac{R_2}{R_1} = 4 \times 4 = 16$$

$$\Rightarrow R_2 = 16 \times 3 = 48\Omega$$

**2. CAPACITANCE:**

Capacitance is the property of capacitor which opposes the sudden change in voltage.

$$Q \propto V$$

$$Q = CV$$

$$\frac{dQ}{dt} = C \frac{dv}{dt}$$


$$I = C \frac{dv}{dt}$$

$$\text{Or, } V = \frac{1}{C} \int_{-\infty}^t I dt$$

The circuit element that stores energy in an electric field is called capacitor.

**Key Points:**

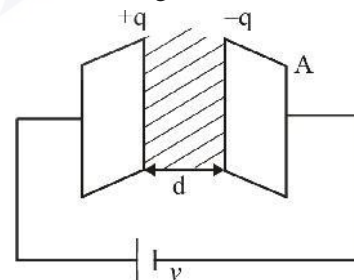- (a) **Capacitors retain the charge & thus electric field** after removal of the source applied. (While inductors do not retain energy). For parallel plate capacitor, the capacitance can be given as:



$$C = \frac{\epsilon_o \epsilon_r A}{d}$$

Where A = cross-sectional area of plate

$\epsilon_r$  = Relative permittivity of dielectric

$\epsilon_o$  = Permittivity of free space

d = distance between plates

$$C = \frac{8.854 \epsilon_r A}{d} pF$$

- (b) The charge q on capacitor results in an electric field in the dielectric which is the mechanism of energy storage.
- (c) Power and energy relation for capacitance are as:


$$P = vi = vc \frac{dv}{dt} = \frac{d}{dt} \left[ \frac{1}{2} cv^2 \right] \quad \left\{ i = \frac{cdv}{dt} \right\}$$

$$P = \frac{d}{dt} \left[ \frac{1}{2} cv^2 \right]$$


$$\text{Energy } w_c = \int P dt = \int vc \frac{dv}{dt} dt$$

- (d) The energy stored in the electric field of capacitance is  $w_c = \frac{1}{2} cv^2$

- (e) Ideal capacitor:

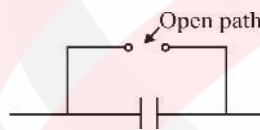

Practical capacitor:

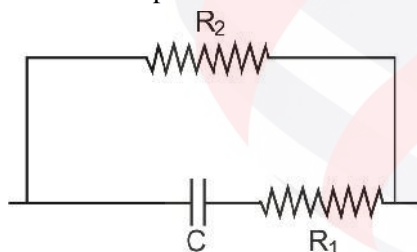

### 3. INDUCTANCE:

**Inductor:-** Inductance is the property of the inductor which opposes the sudden change in current.

**Concept:-** When a time varying current is flowing through the coil, then magnetic flux is induced and it is given by

$$\mathcal{E} \propto I$$

$$\mathcal{E} = Li$$

$$Nw = LI$$

$$L = \frac{Nw}{I}$$

#### Key Points:

- (a) The flux linkage across inductor is  $N\phi$ .

$$\text{Thus } Nw = LI$$

- (b) **Proof of equation A:** According to faraday's law, the emf induced across a inductor is directly proportional to the rate of change of flux through it.

$$e = -N \frac{d\phi}{dt} \quad \{N = \text{no of turns in the coil}\}$$

$$e = -N \frac{d}{dt} \left\{ \frac{LI}{N} \right\}$$

$$e = -L \frac{dI}{dt}$$

-ve sign indicates the opposition caused by induced emf to change of flux (Lenz's Law)

- (c) The power across the inductor is:

$$P = vi = L \frac{di}{dt} i = \frac{d}{dt} \left[ \frac{1}{2} Li^2 \right]$$

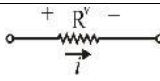
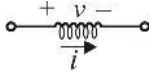

- (d) Energy:  $w = \int P dt = \int Li dt$


$$w = \frac{1}{2} L [i_2^2 - i_1^2]$$

Energy stored in magnetic field by


$$\text{inductor is } w = \frac{1}{2} Li^2$$

**Relationship of parameters:**


Element	Units	Voltage	Current	Power
 Resistance	Ohms (Ω)	$v = Ri$ (ohms law)	$i = \frac{v}{R}$	$P = vi$ $= i^2 R$
 inductance	Henry (H)	$v = L \frac{di}{dt}$	$i = \frac{1}{L} \int v dt$	$P = vi$ $= i \frac{L di}{dt}$
 Capacitance	Farad (F)	$v = \frac{1}{c} \int i dt$	$i = c \frac{dv}{dt}$	$P = vi$ $= v c \frac{dv}{dt}$

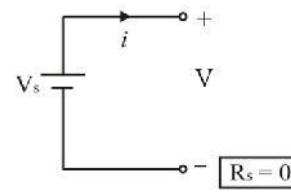

**Ideal Voltage Source**

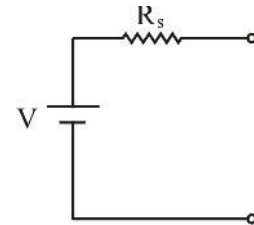

**Practical Voltage source**

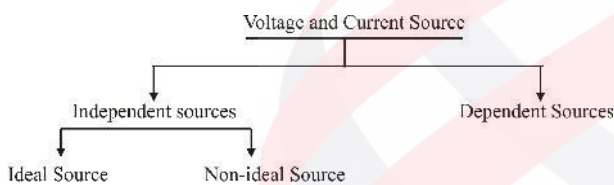

**Voltage & Current Source:**

The sources are of two types, one is independent sources and other is dependent sources:

**Independent sources:**

The voltage or current source in which the value of voltage or current remains constant, and does not vary with other circuit element.

**Ideal & practical voltage sources:**

If the voltage source delivers energy at particular voltage, which is independent of source current then voltage source is ideal, otherwise practical.

Ideal:-  $V = V_S$


Practical:-  $V = V_S - IR_S$

**Ideal & practical voltage current sources:**


If the current source delivers energy at particular value, which is independent of source voltage, then current source is ideal, otherwise practical.

Ideal:  $I = I_S$

Practical:  $I = I_S - V/R_S$

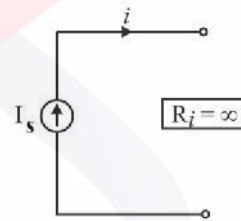


**Ideal current source**

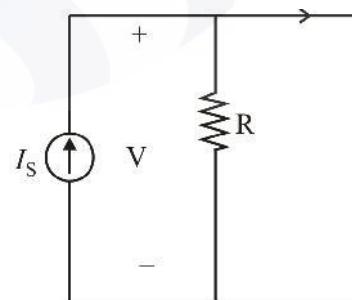


**Practical Current source**

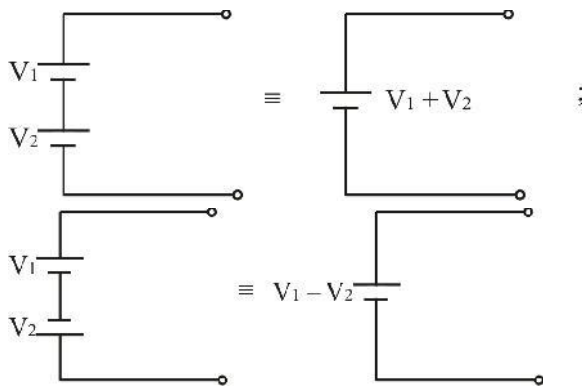
- (a) In non ideal voltage source, the internal resistance of voltage source is of finite value and is always in series with voltage source.
- (b) In non ideal current source, the internal resistance of current source is of finite value & is always in parallel with current source.



(c)

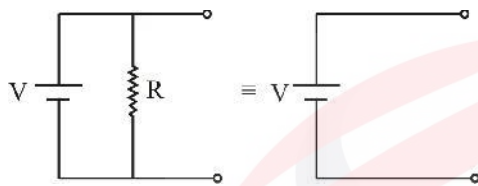

(d)

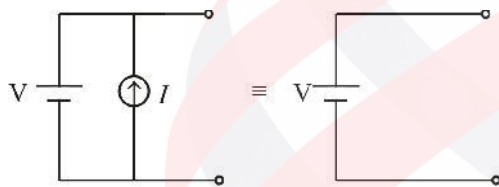


**Key Points:**

- Resistance in parallel with a voltage source is redundant as the terminal voltage remains same.
- Resistance in series with the current source is redundant as the short circuit current in loop is independent of value of R.
- When current sources are connected in series they should all have same value.
- When voltage sources are connected in parallel they should have same value.

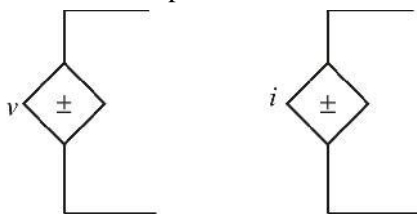
**Dependent Voltage and Current Sources:**

These are voltage and current sources whose value do not remain constant, rather varies with circuit elements or independent sources:



Voltage dependent voltage source

Current dependent voltage source

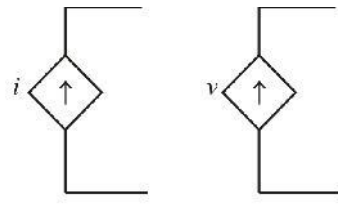

Current dependent current source      Voltage dependent current source

**Distributed and Lumped Network:**

In Lumped network, we can separate resistance, inductance, and capacitance separately or single element in one location is used to represent a distributed resistance.

**Example:** A coil having large number of turns of insulated wire has resistance throughout the length of wire but only resistance at single plane represents the distributed resistance.

**In Distributed network,** the circuit elements are not at one location rather they are distributed.

**Example:** Transmission line, the resistance, inductance and capacitance are distributed throughout the length of Transmission line.

**Note:** In distributed network, the circuit elements are represented as per unit length.

**Non Linearity of circuit elements:**


1. **Resistance Non Linearity:** If the current voltage relationship in an element is not linear, then the element is modeled as non linear resistor.

**Example:** Diode, filament lamp

(a) The non linear resistance can be given as:

$$R = \frac{\Delta V}{\Delta I}$$

Also called as A.C. resistance

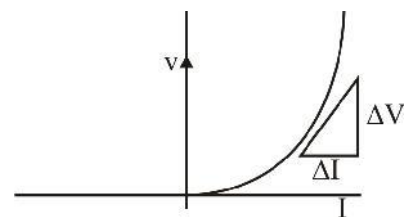

Note: Ohm's law is valid for linear circuit elements. Also it is not valid for open circuit element because for open circuit:

$$I = 0, R = \infty$$


So  $V = \infty$

$$V \neq IR$$

2. **Inductors non linearity:** When the inductance of inductor depends on the current magnitude, then the inductor is called non linear inductor:

Example: Iron core inductor.


**Key points:**

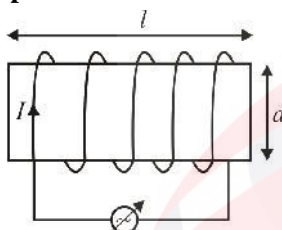

(a)  $NW = LI \Rightarrow L = \frac{NW}{I} = \text{Variable}$

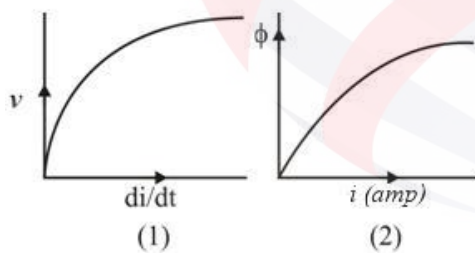(b) Also we know;

$$V = L \frac{di}{dt} \Rightarrow L = \frac{V}{di/dt} = \text{Variable}$$



As the slope of the curve in both cases is **L** (inductance) and **L** is variable. So, the curve is not linear.


The second curve shows that after certain value of current, the flux does not increase due to saturation of iron core.

3. **Nonlinearity in capacitance:** When the capacitance of capacitor depends on voltage

magnitude, then capacitor is called non linear capacitor.

$$Q = CV \Rightarrow C = \frac{Q}{V} = \text{Variable}$$
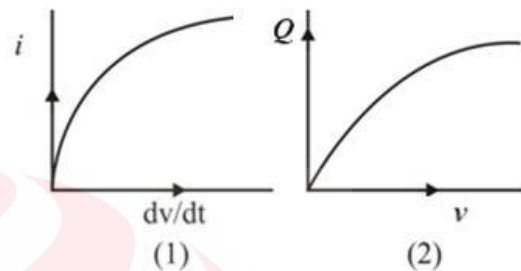
$$i = C \frac{dv}{dt} \Rightarrow C = \frac{i}{dv/dt} = \text{Variable}$$



As the slope of the curve in both cases is **C** and **C** is variable. So, the curve is not linear.

**Key Points:**


(a) Resistances may exhibit non linearity and not obey ohm's law due to thermal effects.

(b) Inductances without air core have saturation characteristics hence they lose their linearity.

**Example:** Obtain the voltage  $V$  in the branch shown in figure for

- (a)  $i_2 = 1A$       (b)  $i_2 = -2A$       (c)  $i_2 = 0A$ .

Solution:  $v = 10 + v_x$  for

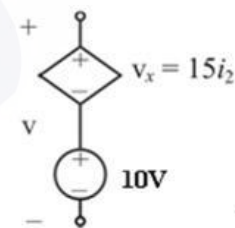

- (a)  $i_2 = 1A$

$$V = 10 + 15 = 25V$$

(b)  $V = 10 - 15 \times 2 = -20V$ .

(c)  $V = 10 + 15 \times 0 = 10V$ .



### SSC-JE PRACTICE SET

1. Ohm's law in point form in field theory can be expressed as

(a)  $V = RI$                       (b)  $J = \frac{E}{\sigma}$                       (c)  $J = \sigma E$                       (d)  $R = \rho \frac{L}{A}$

**Ans.**            (c)

2. Which of the following is a non linear device.

(a) Resistor                      (b) Diode                      (c) Inductor                      (d) Capacitor

**Ans.**            (b)

3. Which of the following is not a bilateral element

(a) Current source                      (b) Resistor

(c) Inductor                      (d) Capacitor

**Ans.**            (a)

4. Consider two metallic wires  $W_1$  and  $W_2$ . They are made up of same material and each has circular cross section. The diameter of  $W_2$  is twice that of  $W_1$  and the length of  $W_2$  is four times that of  $W_1$ . Which one of the following statements is TRUE?

(a) Resistance of  $W_1$  is half that of  $W_2$

(b) Resistance of  $W_1$  is equal to that of  $W_2$

(c) Resistance of  $W_1$  is twice that of  $W_2$

(d) Resistance of  $W_1$  is eight times that of  $W_2$

**ANS: (b)**

**EXP:** Given:  $D_2 = 2D_1$  and  $l_2 = 4l_1$

We know that,

Resistance of wire is given by,

$$R = \frac{\rho l}{A} \quad \{ \dots \rightarrow \text{resistivity} \}$$

$$R = \frac{\rho l}{\frac{f D^2}{4}}$$

$$\Rightarrow R_1 = \frac{\rho l_1}{\frac{f D_1^2}{4}}$$

$$\Rightarrow R_2 = \frac{\rho l_2}{\frac{f D_2^2}{4}} = \frac{\rho 4l_1}{\frac{f 4D_1^2}{4}}$$


$$\Rightarrow R_2 = \frac{4l_1 \rho}{f D_1^2} = R_1$$

5. The series equivalent resistance value in case of a lossy capacitor will be

(a) Very small                      (b) Small                      (c) Large                      (d) None of these

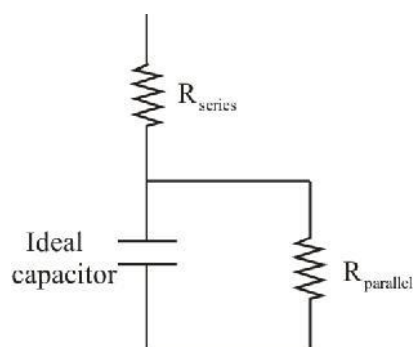**ANS: (b)**

**EXP:** Equivalent circuit for a lossy capacitor:



Here,  $R_{Series}$  is low and  $R_{Parallel}$  is high

6. A capacitor of capacitance  $C_1$  and distance between the plate is  $d_1$ . A second capacitor of capacitance  $C_2$  and distance between the plate is  $d_2$ . When they are connected to series what is the equivalent capacitance?
- (a)  $\frac{d_1 d_2}{d_1 + d_2}$       (b)  $\frac{d_1 + d_2}{d_1 d_2}$       (c)  $C_1 + C_2$       (d)  $\frac{C_1 C_2}{C_1 + C_2}$

**Ans. (d)**

**EXP:** We know that, When two capacitors are in series S. The equivalent capacitance is

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

7. An ideal voltage source should have:
- (a.) Infinite source resistance  
 (b.) Large value of emf  
 (c.) Small value of emf  
 (d.) Zero source resistance

**ANS: d**

8. To neglect a current source, the terminals across the source are
- (a.) Open-circuited  
 (b.) Short-circuited  
 (c.) Replaced by some resistance  
 (d.) Replaced by capacitance

**ANS: a**


9. If two capacitances  $C_1$  and  $C_2$  are connected in parallel then the equivalent capacitance is given by  
**(SSC JE-2015)**

- (a)  $C_1 C_2$       (b)  $\frac{C_1}{C_2}$       (c)  $\frac{C_1 C_2}{C_1 + C_2}$       (d)  $C_1 + C_2$

**Ans: d**



10.

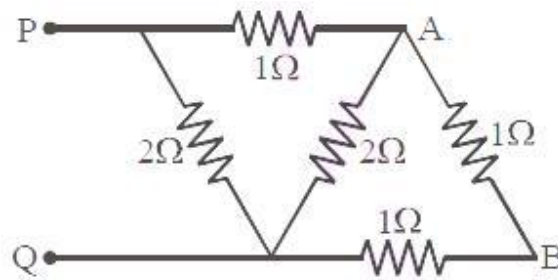

For the circuit shown find the resistance between points P & Q (SSCJE-2015)

- (a)  $1\ \Omega$                       (b)  $2\ \Omega$                       (c)  $3\ \Omega$                       (d)  $4\ \Omega$

Ans: a

11. The rate of change of current in a 4 H inductor is 2 Amps/ sec. Find the voltage across inductor.

- (a) 8 V                      (b) 0.8 V                      (c) 2 V                      (d) 16 V

Ans.(a)

12. How much energy is stored by a 100 mH inductance when a current of 1 A is flowing through it ?

- (a) 0.5 J                      (b) 0.05 J                      (c) 0.005 J                      (d) 5.0 J (SSC-JE-2015)

Ans.(b)

13. What is the Power consumed by the resistor of  $20\ \Omega$  connected across 100 V source ?

- (a) 500 W                      (b) 50 W                      (c) 100 W                      (d) 300 W

Ans.(a)

14. A linear circuit is one whose parameters

- (a) change with change in current                      (b) change with change in voltage (SSC-JE-2015)  
 (c) do not change with voltage and current                      (d) None of the above


Ans. (c)

15. An active element in a circuit is one which

- (a) supplies energy                      (b) receives energy (SSC-JE-2015)  
 (c) dissipates energy                      (d) both receives and supplies energy

Ans. (a)


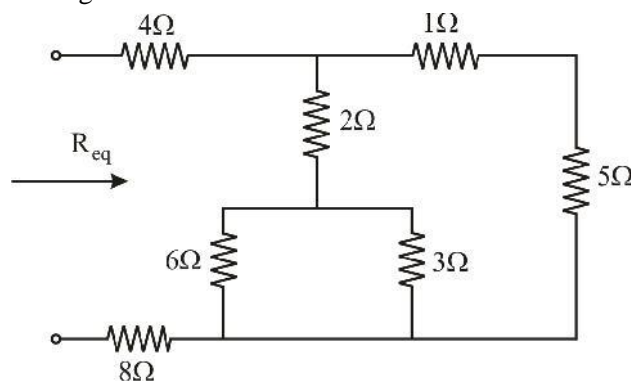
16. The  $R_{eq}$  for the circuit shown in figure is: (SSC-JE-2014)



- (a)  $14.4\ \Omega$                       (b)  $14.57\ \Omega$                       (c)  $15.27\ \Omega$                       (d)  $15.88\ \Omega$

ANS: a

EXP:

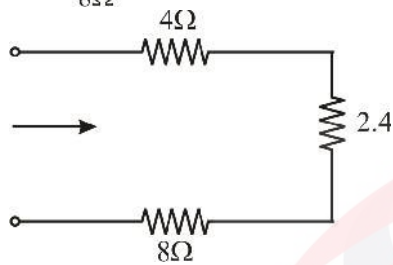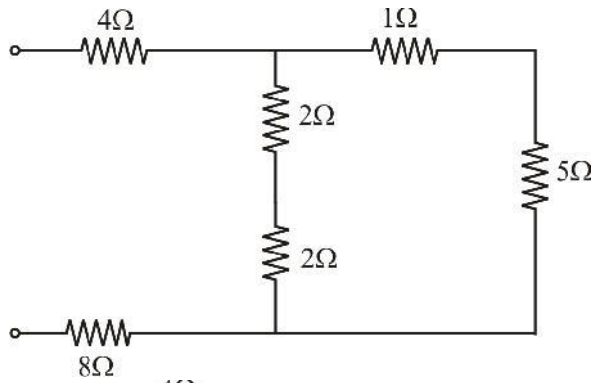


$$R_{eq} = 4 + 8 + 2.4 = 14.4$$

17. The SI unit of conductivity is: (SSCJE-2014)  
 (a) ohm-m (b) ohm/m (c) mho-m (d) mho/m

ANS: d

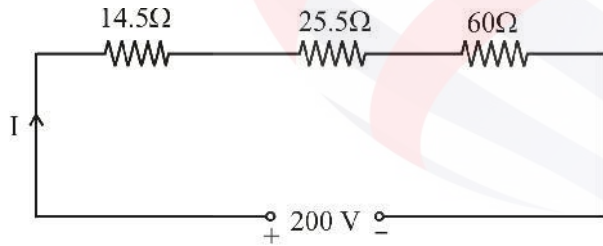18. Calculate the voltage drop across 14.5Ω resistance (SSCJE-2014)



- (a) 14.5V (b) 18V (c) 29V (d) 30.5V

ANS: c

EXP: 
$$V = \frac{14.5}{14.5 + 25.5 + 60} \times 200 = 29 \text{ V}$$